



Nombres de estudiantes:

Jesus Alberto Beato Pimentel.

Matriculas:

2023-1283.

Institución académica:

Instituto Tecnológico de las Américas (ITLA).

Materia:

Circuitos Eléctricos II

Profesor:

Ing. Omar De Los Santos Bueno

Tema del trabajo:

Ejercicios pautados del cap. 13



PROBLEMAS

SECCIÓN 13.2 Teorema de superposición

1. Por medio de superposición, determine la corriente a través de la inductancia X_L en la red de la figura 13.105.

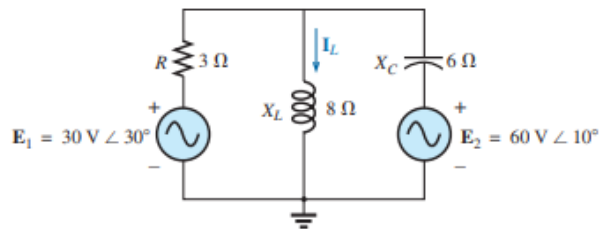


FIG. 13.105
Problema 1.

Handwritten solution for Problem 1 using the superposition theorem.

Initial circuit parameters:

- $Z_1 = 3 \Omega \angle 0^\circ$
- $Z_2 = 8 \Omega \angle 90^\circ$
- $Z_3 = 6 \Omega \angle -90^\circ$
- $E_1 = 30 \text{ V} \angle 30^\circ$
- $E_2 = 60 \text{ V} \angle 10^\circ$

Step 1: Current I_1 due to E_1 only.

When E_2 is replaced by a short circuit, the circuit consists of E_1 in series with Z_1 and a parallel combination of Z_2 and Z_3 .

$$Z_3 = Z_2 \cdot Z_3 = \frac{(8 \Omega \angle 90^\circ)(6 \Omega \angle -90^\circ)}{(8 \Omega \angle 90^\circ) + (6 \Omega \angle -90^\circ)} = 24 \Omega \angle -90^\circ$$

$$Z_2 + Z_3 = (8 \Omega \angle 90^\circ) + (6 \Omega \angle -90^\circ)$$

$$I = \frac{E_1}{Z_1 + Z_3} = \frac{30 \text{ V} \angle 30^\circ}{(3 \Omega \angle 0^\circ) + (24 \Omega \angle -90^\circ)} = \frac{30 \angle 30^\circ}{24.19 \Omega \angle -82.87^\circ} = 1.24 \text{ A} \angle 112.88^\circ$$

The current through the inductor Z_2 is:

$$I' = \frac{Z_3 \cdot I}{Z_2 + Z_3} = \frac{(6 \Omega \angle -90^\circ)(1.24 \text{ A} \angle 112.88^\circ)}{(8 \Omega \angle 90^\circ) + (6 \Omega \angle -90^\circ)} = \frac{7.44 \text{ V} \angle 22.88^\circ}{2 \Omega \angle 90^\circ} = 3.72 \text{ A} \angle -67.13^\circ$$

Step 2: Current I'' due to E_2 only.

When E_1 is replaced by a short circuit, the circuit consists of E_2 in series with Z_3 and a parallel combination of Z_1 and Z_2 .

$$Z_1 \cdot Z_2 = \frac{(3 \Omega \angle 0^\circ)(8 \Omega \angle 90^\circ)}{(3 \Omega \angle 0^\circ) + (8 \Omega \angle 90^\circ)} = 24 \Omega \angle 90^\circ$$

$$Z_1 + Z_2 = \frac{(3 \Omega \angle 0^\circ)(8 \Omega \angle 90^\circ)}{(3 \Omega \angle 0^\circ) + (8 \Omega \angle 90^\circ)} = 2.81 \Omega \angle 20.56^\circ$$

$$I = \frac{E_2}{Z_3 + Z_6} = \frac{60 \text{ V} \angle 10^\circ}{(6 \Omega \angle -90^\circ) + (2.81 \Omega \angle 20.56^\circ)} = \frac{60 \text{ V} \angle 10^\circ}{5.66 \Omega \angle -62.31^\circ} = 10.60 \text{ A} \angle 72.31^\circ$$

The current through the inductor Z_2 is:

$$I'' = \frac{Z_1 \cdot I}{Z_1 + Z_2} = \frac{(3 \Omega \angle 0^\circ)(10.60 \text{ A} \angle 72.31^\circ)}{(3 \Omega \angle 0^\circ) + (8 \Omega \angle 90^\circ)} = \frac{31.8 \text{ V} \angle 72.31^\circ}{8.54 \Omega \angle 69.44^\circ} = 3.72 \text{ A} \angle 2.87^\circ$$

Final result:

$$I_{XL} = I' + I''$$

$$I_{XL} = (3.72 \text{ A} \angle -67.13^\circ) + (3.72 \text{ A} \angle 2.87^\circ)$$

$$I_{XL} = 6.09 \text{ A} \angle -32.13^\circ$$

2. Por medio de superposición, determine la corriente a través de la capacitancia X_C en la red de la figura 13.106.

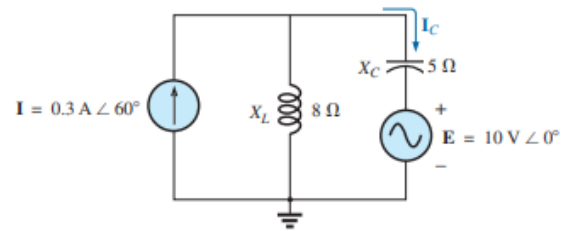


FIG. 13.106
Problema 2.

②

$I = 0.3 \text{ A} \angle 60^\circ$
 $X_L = 8 \Omega$
 $X_C = 5 \Omega$
 $E = 10 \text{ V} \angle 0^\circ$

$Z_1 = 8 \Omega \angle 90^\circ$
 $Z_2 = 5 \Omega \angle -90^\circ$
 $E = 10 \text{ V} \angle 0^\circ$
 $I = 0.3 \text{ A} \angle 60^\circ$

$I' = \frac{Z_1 \cdot I}{Z_1 + Z_2} = \frac{(8 \Omega \angle 90^\circ)(0.3 \text{ A} \angle 60^\circ)}{(8 \Omega \angle 90^\circ) + (5 \Omega \angle -90^\circ)}$
 $I' = \frac{2.4 \text{ V} \angle 150^\circ}{3 \Omega \angle 90^\circ}$
 $I' = 0.8 \text{ A} \angle 60^\circ$

$I'' = \frac{E}{Z_1 + Z_2} = \frac{10 \text{ V} \angle 0^\circ}{(8 \Omega \angle 90^\circ) + (5 \Omega \angle -90^\circ)}$
 $I'' = \frac{10 \text{ V} \angle 0^\circ}{3 \Omega \angle 90^\circ}$
 $I'' = 3.33 \text{ A} \angle -90^\circ$

$I_{X_C} = I' - I''$
 $I_{X_C} = (0.8 \text{ A} \angle 60^\circ) - (3.33 \text{ A} \angle -90^\circ)$
 $I_{X_C} = 4.04 \text{ A} \angle 84.32^\circ$

13. Determine el circuito equivalente de Thévenin para la parte de la red de la figura 13.117 externa a los elementos entre los puntos a y b .

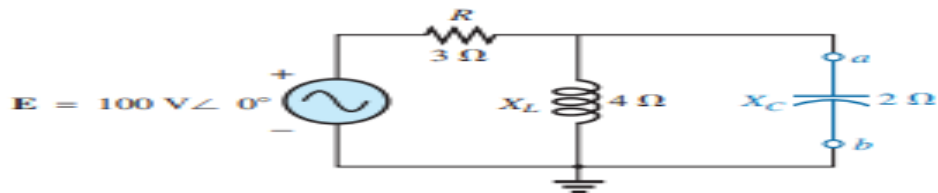


FIG. 13.117
Problemas 13 y 30.

1a

$Z_1 = 3\Omega \angle 0^\circ$
 $Z_2 = 4\Omega \angle 90^\circ$
 $E = 100V \angle 0^\circ$

$Z_{th} = \frac{Z_1 \cdot Z_2}{Z_1 + Z_2} = \frac{(3\Omega \angle 0^\circ)(4\Omega \angle 90^\circ)}{(3\Omega \angle 0^\circ) + (4\Omega \angle 90^\circ)} = \frac{12\Omega \angle 90^\circ}{5\Omega \angle 53.13^\circ}$
 $Z_{th} = 2.4\Omega \angle 36.87^\circ$

$E_{th} = \frac{Z_2 \cdot E}{Z_2 + Z_1} = \frac{(4\Omega \angle 90^\circ)(100V \angle 0^\circ)}{(3\Omega \angle 0^\circ) + (4\Omega \angle 90^\circ)} = \frac{400 \angle 90^\circ}{5\Omega \angle 53.13^\circ}$
 $E_{th} = 80V \angle 36.87^\circ$

The final Thévenin equivalent circuit consists of a voltage source $E_{th} = 80V \angle 36.87^\circ$ in series with a resistor $Z_{th} = 2.4\Omega \angle 36.87^\circ$, connected to terminals a and b .

30. Determine el circuito equivalente de Norton de la red externa para los elementos entre a y b para la red de la figura 13.117.


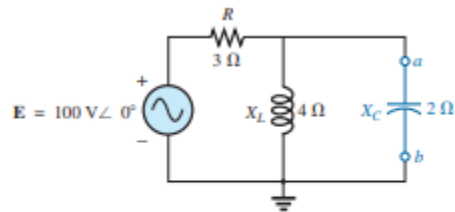


FIG. 13.117
Problemas 13 y 30.

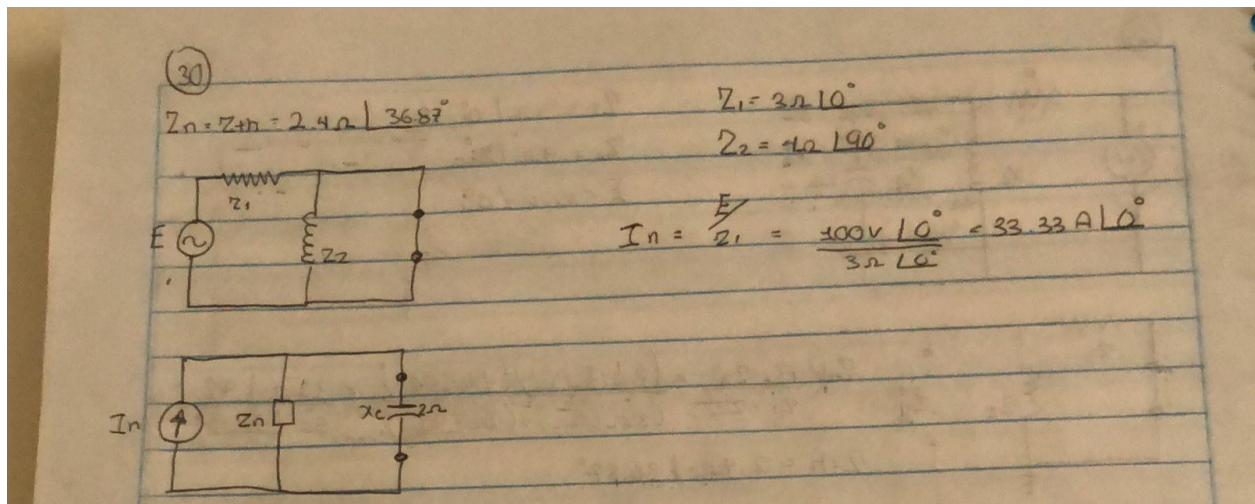

31. Determine el circuito equivalente de Norton de la red externa para los elementos entre a y b para la red de la figura 13.119.


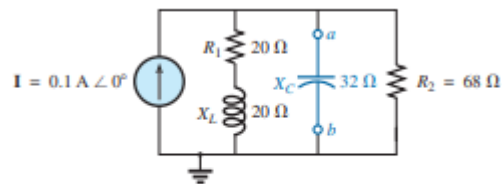


FIG. 13.119
Problemas 15 y 31.

31

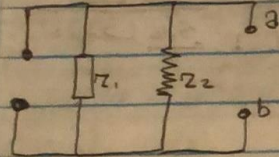


$$Z_1 = 20\Omega + j20\Omega \rightarrow 28.28\Omega / 45^\circ$$

$$Z_2 = 68\Omega / 0^\circ$$

$$Z_n = \frac{Z_1 \cdot Z_2}{Z_1 + Z_2} = \frac{(28.28 / 45^\circ)(68\Omega / 0^\circ)}{(28.28 / 45^\circ) + (68\Omega / 0^\circ)}$$

$$Z_n = \frac{1923.04\Omega}{90.24\Omega / 12.80^\circ}$$
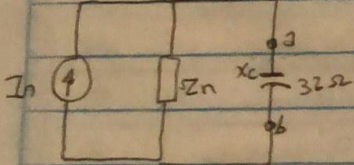
$$Z_n = 21.31\Omega / 32.2^\circ$$


$$I_n = 0.14 / 0^\circ$$

*33. Determine el circuito equivalente de Norton para la parte de la red de la figura 13.126 externa a los elementos entre los puntos a y b.


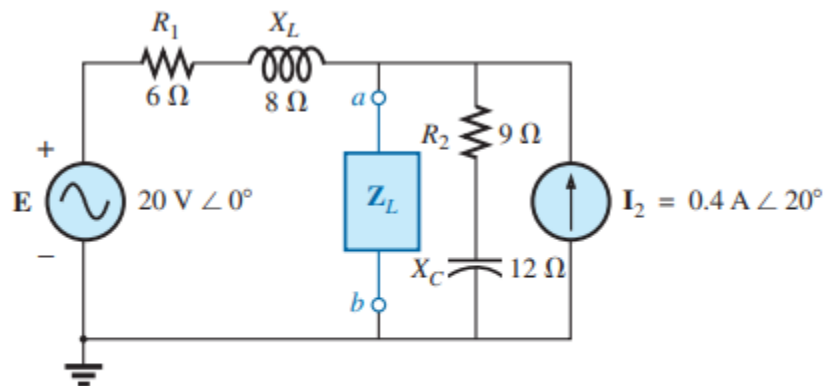


FIG. 13.126
Problema 33.

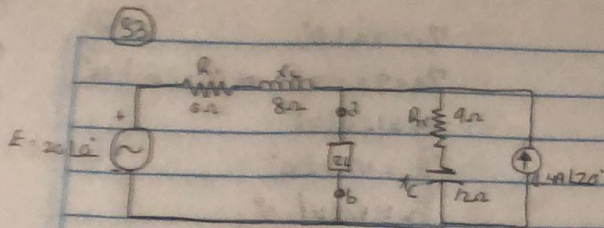


$$Z_1 = 6\Omega + j8\Omega \rightarrow 10\Omega / 53.13^\circ$$

$$Z_2 = 4\Omega + j12\Omega \rightarrow 12.65\Omega / 71.57^\circ$$

$$I = 20\angle 0^\circ$$


$$I = 0.4A / 20^\circ$$

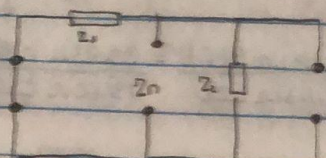


$$Z_N = \frac{Z_1 \cdot Z_2}{Z_1 + Z_2} = \frac{(10\Omega / 53.13^\circ)(12.65\Omega / 71.57^\circ)}{(10\Omega / 53.13^\circ) + (12.65\Omega / 71.57^\circ)}$$

$$Z_N = \frac{150\Omega / 0^\circ}{15.52\Omega / 14.93^\circ}$$

$$Z_N = 9.66\Omega / 14.93^\circ$$

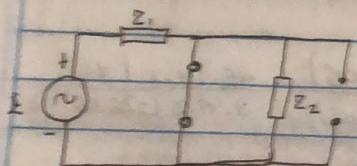
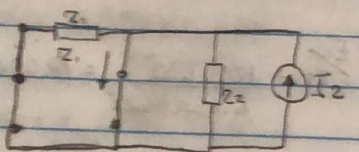
$$I' = \frac{E}{Z_1} = \frac{20\angle 0^\circ}{10\Omega / 53.13^\circ} = 2A / -53.13^\circ$$




$$I'' = 0.4A / 20^\circ$$

$$I_N = I' + I''$$

$$I_N = (2A / -53.13^\circ) + (0.4A / 20^\circ)$$

$$I_N = 2.15A / -42.88^\circ$$

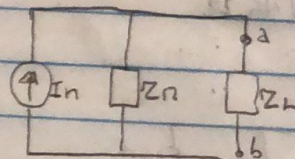

34. Determine el circuito equivalente de Norton para la parte de la red de la figura 13.127 externa a los elementos entre los puntos a y b.

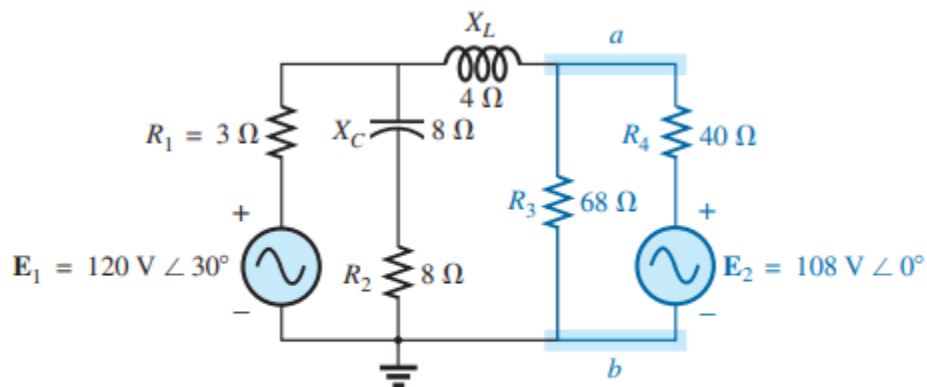


FIG. 13.127
Problema 34.

Handwritten solution for Problem 34:

34

$Z_1 = 3 \Omega \angle 0^\circ$
 $Z_2 = 8 \Omega - j8 \Omega \rightarrow 11.31 \Omega \angle -45^\circ$
 $Z_3 = 4 \Omega \angle 90^\circ$
 $E_1 = 120 V \angle 30^\circ$
 $E_2 = 108 V \angle 0^\circ$

$Z_a = \frac{Z_1 \cdot Z_2}{Z_1 + Z_2} = \frac{(3 \Omega \angle 0^\circ)(11.31 \Omega \angle -45^\circ)}{(3 \Omega \angle 0^\circ) + (11.31 \Omega \angle -45^\circ)} = \frac{33.93 \Omega \angle -45^\circ}{13.60 \Omega \angle -36.02^\circ}$
 $Z_a = 2.49 \Omega \angle -8.98^\circ$
 $Z_n = Z_a + Z_3$
 $Z_n = (4 \Omega \angle 90^\circ) + (2.49 \Omega \angle -8.98^\circ) = 4.37 \Omega \angle 55.74^\circ$

$Z_b = \frac{Z_2 \cdot Z_3}{Z_2 + Z_3} = \frac{(11.31 \Omega \angle -45^\circ)(4 \Omega \angle 90^\circ)}{(11.31 \Omega \angle -45^\circ) + (4 \Omega \angle 90^\circ)} = \frac{45.24 \Omega \angle 45^\circ}{8.94 \Omega \angle -26.56^\circ}$
 $Z_b = 5.06 \Omega \angle 71.56^\circ$

$Z_T = Z_1 + Z_b$
 $Z_T = (3 \Omega \angle 0^\circ) + (5.06 \Omega \angle 71.56^\circ)$
 $Z_T = 6.65 \Omega \angle 46.22^\circ$

$I = \frac{E_1}{Z_T} = \frac{120 V \angle 30^\circ}{6.65 \Omega \angle 46.22^\circ} = 18.05 A \angle -16.22^\circ$

$I_n = \frac{Z_3 I}{Z_2 + Z_3} = \frac{(11.31 \Omega \angle -45^\circ)(18.05 A \angle -16.22^\circ)}{(11.31 \Omega \angle -45^\circ) + (4 \Omega \angle 90^\circ)}$
 $I_n = \frac{204.15 V \angle -61.22^\circ}{8.94 \Omega \angle -26.56^\circ}$
 $I_n = 22.84 A \angle -34.66^\circ$

Final circuit diagram showing the Norton equivalent circuit with current source I_n in parallel with Z_n and Z_b in series.

SECCIÓN 13.5 Teorema de transferencia de potencia máxima

44. Determine la impedancia de carga Z_L para la red de la figura 13.129 para el suministro de potencia máxima a la carga, y determine la potencia máxima suministrada a la carga.

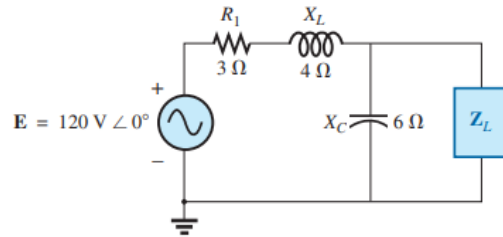


FIG. 13.129
Problema 44.

(44)

$E = 120V \angle 0^\circ$
 $Z_1 = 3\Omega + j4\Omega = 5\Omega \angle 53.13^\circ$
 $Z_2 = 6\Omega \angle -90^\circ$
 $E = 120V \angle 0^\circ$

$Z_{th} = \frac{Z_1 \cdot Z_2}{Z_1 + Z_2} = \frac{(5\Omega \angle 53.13^\circ)(6\Omega \angle -90^\circ)}{(5\Omega \angle 53.13^\circ) + (6\Omega \angle -90^\circ)} = \frac{30\Omega \angle -36.87^\circ}{3.61\Omega \angle -33.69^\circ}$
 $Z_{th} = 8.31\Omega \angle -3.18^\circ$

$E_{th} = \frac{(6\Omega \angle -90^\circ)(120V \angle 0^\circ)}{(5\Omega \angle 53.13^\circ) + (6\Omega \angle -90^\circ)} = \frac{720V \angle -90^\circ}{3.61\Omega \angle -33.69^\circ} = 199.45V \angle -56.31^\circ$

$P_{max} = \frac{E_{th}^2}{4Z_{th}} = \frac{(199.45V)^2}{4(8.31\Omega)}$
 $P_{max} = \frac{39780.30V}{33.24\Omega}$
 $P_{max} = 1196.76W$

- *46. Determine la impedancia de carga Z_L para la red de la figura 13.131 para el suministro de potencia máxima a la carga y determine la potencia máxima suministrada a la carga.

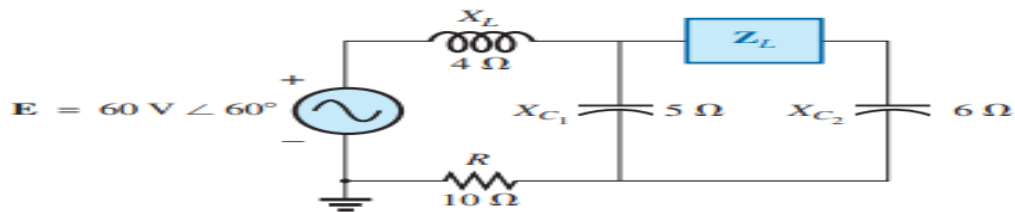


FIG. 13.131
Problema 46.

46

$Z_1 = 4 \Omega \angle 90^\circ$
 $Z_2 = 10 \Omega \angle 0^\circ$
 $Z_3 = 5 \Omega \angle -90^\circ$
 $Z_4 = 6 \Omega \angle -90^\circ$
 $E = 60 V \angle 60^\circ$

$Z_a = Z_1 + Z_2 = (4 \Omega \angle 90^\circ) + (10 \Omega \angle 0^\circ) = 10.77 \Omega \angle 26.8^\circ$
 $Z_b = Z_3 + Z_4 = (5 \Omega \angle -90^\circ) + (6 \Omega \angle -90^\circ) = 11 \Omega \angle -90^\circ$

$Z_{Th} = \frac{Z_a \cdot Z_b}{Z_a + Z_b} = \frac{(10.77 \angle 26.8^\circ)(11 \angle -90^\circ)}{(10.77 \angle 26.8^\circ) + (11 \angle -90^\circ)} = \frac{118.47 \angle -63.2^\circ}{12.21 \angle -34.99^\circ}$
 $Z_{Th} = 9.70 \Omega \angle -28.2^\circ \rightarrow 2.48 \Omega - j4.75 \Omega$

$E_{Th} = \frac{Z_2 E}{Z_2 + Z_1 + Z_2} = \frac{(5 \Omega \angle -90^\circ)(60 V \angle 60^\circ)}{(5 \Omega \angle -90^\circ) + (4 \Omega \angle 90^\circ) + (10 \Omega \angle 0^\circ)}$
 $E_{Th} = \frac{300 V \angle -30^\circ}{10.05 \angle 5.31^\circ}$
 $E_{Th} = 29.85 V \angle -24.29^\circ$

$$P_{max} = \frac{E_{Th}^2}{4Z_{Th}} = \frac{(29.85 V)^2}{4(2.48 \Omega)}$$

$$P_{max} = \frac{891.02 V}{9.90 \Omega}$$

$$P_{max} = 90.00 W$$